

**PURBANCHAL UNIVERSITY**

**III SEMESTER FINAL EXAMINATION-2006**

**LEVEL:** B. E. (Computer/Electronics & Communication)

**SUBJECT:** BEG223EL, Electrical Engineerin-II

**Full Marks:** 80

**TIME:** 03:00 hrs.

**Pass Marks:** 32

Candidates are required to give their answers in their own words as far as practicable.

All questions carry equal marks. The marks allotted for each sub-questions is specified along its side.

**Attempt any FIVE questions**

Q. [1] [a] Generate the matrix mode for the network in Fig. 1[a] using nodal analysis. And hence obtain the solution for the network using Cramer's Rule if  $R_1 = 4\Omega$ ,  $R_2 = 2\Omega$ ,  $R_m = 4\Omega$ ,  $\alpha = 0.4$ ,  $\beta = 0.2$ ,  $V = 24$  volts,  $I = 10$  Amp.

Figure:

[b] In the given circuit, Fig 1[b], switch  $K$  is closed at  $t=0$ , the steady state condition having reached previously. Obtain the expression for the current in the circuit at any time  $t$ .  
If  $R_1 = R_2 = 100\Omega$ ,  $V = 10$ volts and  $L = 1$ H, Calculate the following at time  $t = 5$ ms.

- (i) Current.
- (ii) Voltage drop across  $R_2$ .
- (iii) Voltage across  $L$ .

Q. [2] [a] In the series RL circuit shown in Fig. 2[a] the input  $V(t) = 10\sin(10t + \pi/6)$  is applied at time  $t=0$ . Obtain the particular solution for the circuit current  $i(t)$ . Assume zero initial current through the inductor  $L$ . [8]

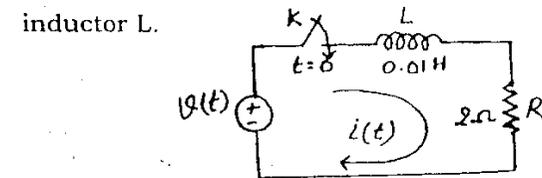


Fig. 2 [a]

[b] State and prove the initial and final value theorem for Laplace Transform. [8]

Q. [3] [a] An exponential voltage  $v(t) = 6e^{-2t}$  is applied at  $t=0$  to a series RLC circuit with resistor  $R=5\Omega$ , inductor  $L=1$ H and capacitor  $C=0.25\mu F$ . Obtain the complete solution for the current  $i(t)$  in the circuit using Laplace transformation. Assume zero initial condition before the application of the voltage. [6]

[b] Define the terms: Transfer function, voltage and current transfer ratio, transfer admittance and transfer impedance. [4]

[c] The transform current  $I(s)$  in a network is given the following response. [6]

$$I(s) = \frac{2S}{(S+1)(S+2)}$$

Plot the poles & zeros in S-plane and hence obtain the time-domain response. [6]

- Q. [4] [a] The current in an inductance  $L=0.01H$  has a waveform as shown in Fig. 4 [a]. Obtain the trigonometric Fourier series for the voltage across the inductance  $V_L$ . Take  $\omega = 500\text{rad/s}$ . [8]

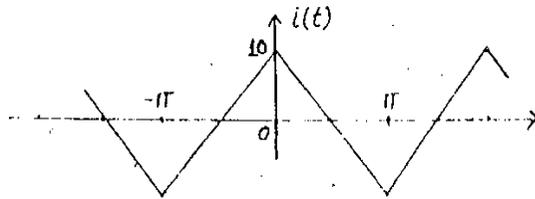


Fig. 4[a].

- [b] The given network shown in Fig. 4[b] is driven by a current source and is terminated by resistor  $R_2$  at port 2. For this network calculate  $G_{21}(s)$ ,  $\alpha_{21}(s)$ ,  $Z_{21}(s)$ ,  $Y_{21}(s)$  and  $z_{11}(s)$ ,  $Y_{11}(s)$  and  $Z_{11}(s)$ . [8]

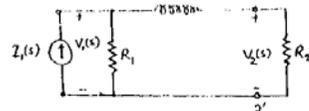


Fig. 4[b]

- Q. [5] [a] Sketch the Bode plot (magnitude and phase) for the following network function.

$$H(s) = \frac{(1+0.2S)(1+0.025s)}{s^2(1+0.005s)(1+0.001s)}$$

- [b] Define reciprocal network. For a reciprocal network show that  $AD-BC=1$ ,  $A, B, C, D$  are transmission parameters. [4]

- Q. [6] [a] The network of the Fig. 6(a) is the type used for the so-called "notch filter". For the element values that are given, determine the y parameters. [10]

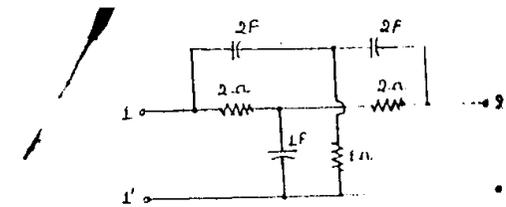


Fig. 6[a]

- [b] Realize a network whose impedance is given as: [6]

$$z(s) = \frac{s(s^2 + 4)}{2(s^2 + 1)(s^2 + 9)}$$


**PURBANCHAL UNIVERSITY**  
**III SEMESTER FINAL EXAMINATION-2005**  
**LEVEL: B. E. (Computer/Electronics & Communication)**  
**SUBJECT: BEG223EL, Electrical Engineering-II**  
**Full Marks: 80**  
**Pass Marks: 32**  
**TIME: 03:00 hrs.**

Candidates are required to give their answers in their own words as far as practicable.


All questions carry equal marks. The marks allotted for each sub-questions is specified along its side.

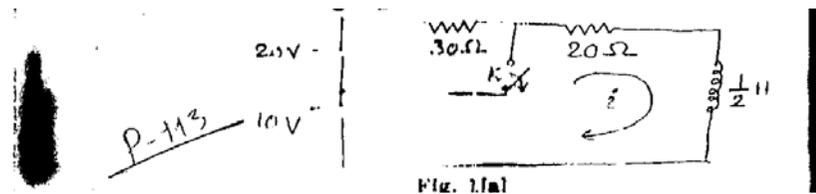**Attempt any FIVE questions**


Q. [1] [a] The network of Fig. 1[a] reaches a steady state with the switch K open. At t=0, switch k is closed. Find i(t) for the numerical values given for the element, sketch the current waveform, and indicate the value of the time constant.



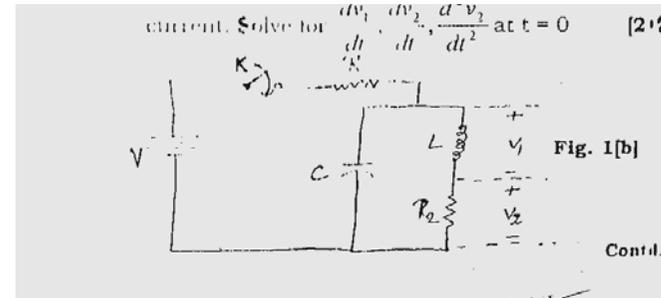
[b] In the network of Fig. 1[b], the switch k is closed at t = 0 with zero capacitor voltage and zero inductor current. Solve for  $\frac{dv_1}{dt}$ ,  $\frac{dv_2}{dt}$ ,  $\frac{d^2v_2}{dt^2}$  at t = 0. [2+2+2]



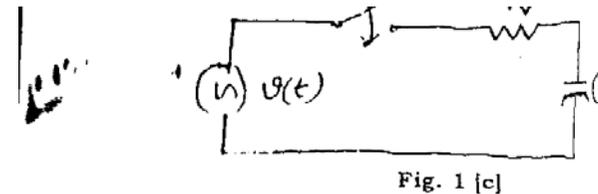[c] Find the complete response of RC series circuit shown in Fig. 1[c] to sinusoidal input  $V \sin \omega t$ . [5]



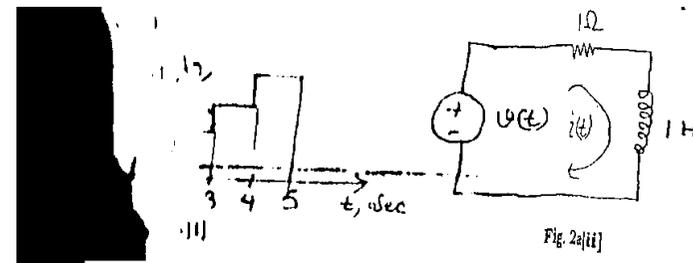Q. [2] [a] The voltage v(t) as shown in figure Fig. 2 [a(i)], is applied to R-L network of Fig. 2 [a(ii)]. Find the current i(t). [8]



[b] In the network shown in Fig. 2[b], the switch K is closed at  $t=0$  with the network previously unenergised. For the element values shown on the diagram, find  $i_1(t)$  and  $i_2(t)$  using Laplace transformation method. [8]

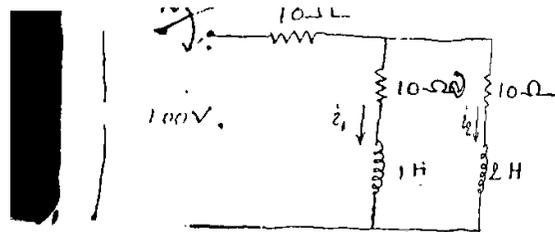


Fig. 2[b]

Contd. ...

- Q. [3] [a] For the Laplace transformation  $I(s) = \frac{2s+10}{s(s+2)}$ , determine the value of  $i(0^+)$  and  $i(\infty)$  making use of initial value theorem and final value theorem. [2+2]
- [b] Find the range of  $K$  such that the network with the characteristics equation:  $S^4+s^2+4s^2+Ks+3=0$  is stable [6]
- [c] Find the driving point impedance of the network shown in Fig. 3[c]. Also find poles and zeroes of the network and locate them in the  $s$ -plane. [6]

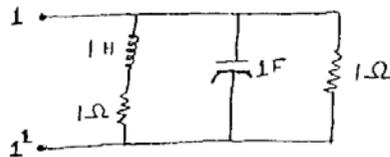


Fig. 3 [c]

- Q. [4] [a] Find the Fourier Series expansion of the continuous waveform shown in fig. 4(a).

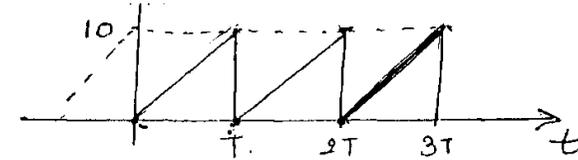


Fig. 4[a]

- [b] Show that for the two port network, under the condition of reciprocity  $\Delta T = AD - BC = 1$  in terms of transmission parameters. [5]
- [c] Write down the properties of RL networks. [3]
- Q. [5] [a] For the two port network of the fig 5[a]. [3+3+6]
- [i] Determine the voltage ratio transfer function  $\frac{V_2(s)}{V_1(s)}$ .
- [ii] Find the expression for half-power frequency.


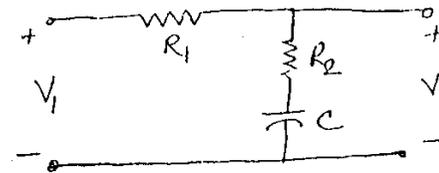


Fig. 5[a]

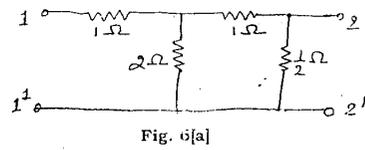- [b] Sketch the (asymptotic) Bode plot (Magnitude and Phase) for the network whose transfer function is given as: [10]
- Q. [6] [a] Determine the Y and z parameters of the circuit shown in Fig. 6[a].



[b] Synthesize the given function:

$$Y(s) = \frac{s^3 + 2s^2 + 3s + 1}{s^3 + s^2 + 2s + 1}$$

**PURBANCHAL UNIVERSITY**

**III SEMESTER BACK-PAPER EXAMINATION-2005**

**LEVEL:** B. E. (Computer/Electronics & Communication)

**SUBJECT:** BEG223EL, Electrical Engineering-II

**Full Marks:** 80

**Pass Marks:** 32


**TIME:** 03:00 hrs.

Candidates are required to give their answers in their own words as far as practicable.

All questions carry equal marks. The marks allotted for each sub-questions is specified along its side.

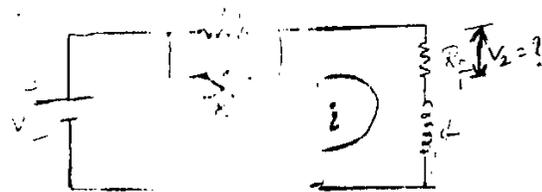
**Attempt any FIVE questions**

Q. [1] [a] In the given circuit of fig. 1[a] switch k is closed at time  $t = 0$ , the steady state is being reached previously. Calculate the current I following through the circuit and the voltage across R2 and L at time  $t = 5\text{ms}$ . If the applied voltage is 10vots.  $R_1 = R_2 = 100\text{ ohm}$  and  $L = 1\text{H}$ .




[b] Calculate the following for the network of fig 1[b] when switch is closed at  $t = 0$ . [2+3+3]

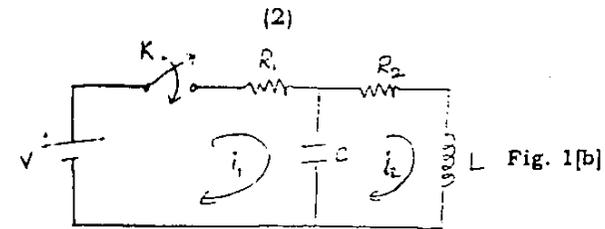- [i]  $i_1(0+)$ ,  $i_2(0+)$  [ii]  $di_1/dt(0+)$ ,  $di_2/dt(0+)$
- [iii]  $d^2i_1/dt^2(0+)$ ,  $d^2i_2/dt^2(0+)$




[c] Define active and passive network. [2]

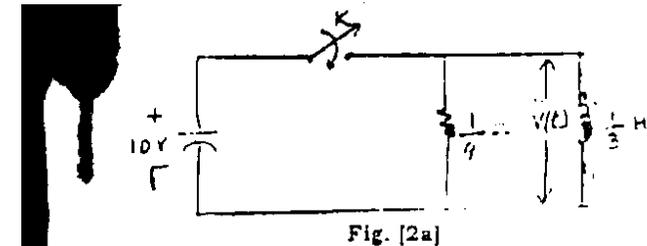Q. [2] [a] In the given circuit of fig [2a], capacitor C has an initial voltage  $V_c(0+) = 10\text{v}$  and at the same instant current in the inductor is zero switch k is closed at time  $t = 0$ . Obtain expression for the voltage  $v(t)$  across the inductor L.



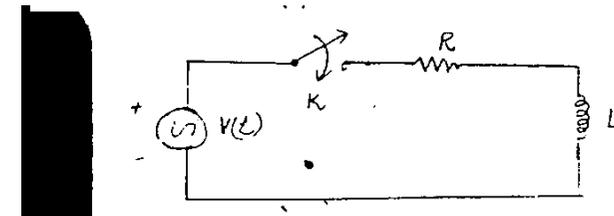[b] Find the complete response of RL series circuit shown in fig. 2[b] to sinusoidal input  $V\sin\omega t$ . [5]



[c] Derive the first shifting theorem using Laplace transform. [4]

Q. [3] [a] plot the pole and zero in the s-plane and hence obtain the time domain responses of the given transformed circuit in a network. [6]

$$I(s) = \frac{2S}{(s+1)(s+2)}$$

[b] Find the range of B such that the network with the characteristics equation: [6]

$$S^4 + 3s^3 + 3s^2 + 2s + k = 0 \text{ is stable.}$$

[c] Define unit step function, dirac delta functions, ramp function and transfer function. [4]

Q. [4] [a] Find the Fourier series expansion of the square waveform shown in fig. 4[a]. [8]

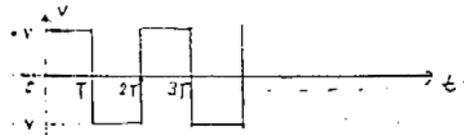


Fig. 4[a]

[b] Under what condition for the two port network is  $z_{12} = z_{21}$  ? Show it analytically in terms of z parameters. [5]

[c] Define positive real function and write its properties. [3]

Q. [5] [a] Find the voltage ratio transfer functions  $V_2(s)/V_1(s)$  of a given two port network shown in fig 5[a]. [6]

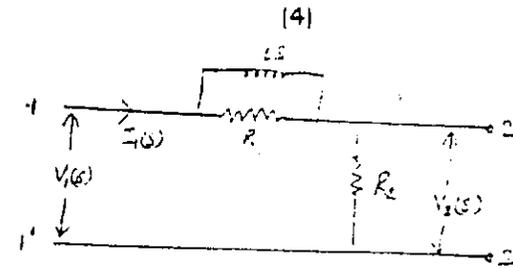


Fig. 5[a]

[b] Sketch the bode plot magnitude and phases for the network whose transfer function is given as:

$$G(s) = \frac{10}{3(1 - 0.5S)(1 - 0.1S)}$$

Q. [6] [a] Determine the hybrid parameters of the circuit shown in fig 6[a].

Figure:

[b] Synthesize the given parameter.

$$Z(s) = \frac{S^2 + 2S + 8}{S(S + 3)}$$

[c] Write short note on: [2×2=4]

- [i] Ideal and non-ideal filters.
- [ii] Transmission parameters.


**PURBANCHAL UNIVERSITY**  
**III SEMESTER FINAL EXAMINATION-2004**  
**LEVEL: B. E. (Computer/Electronics & Communication)**  
**SUBJECT: BEG223EL, Electrical Engineering-II**  
**Full Marks: 80**  
**Pass Marks: 32**  
**TIME: 03:00 hrs.**

Candidates are required to give their answers in their own words as far as practicable.

All questions carry equal marks. The marks allotted for each sub-questions is specified along its side.

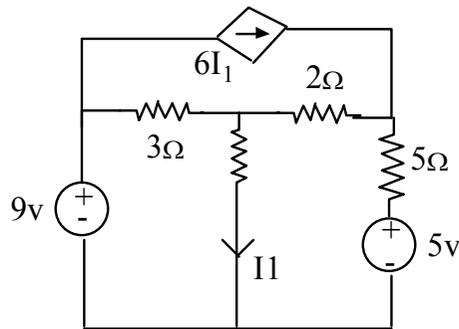
**Attempt any FIVE questions**

Q. [1] [a] Find the current I in the circuit shown in fig 1[a]. [6]




[b] Obtain the expression for voltage across the capacitor when a series R-C circuit is excited by a d.c . Excitation of voltage V. [5]

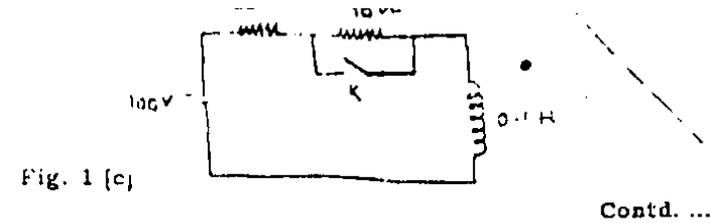
[c] Obtain the complete expression for current when the switch K is closed at t=0 in fig. 1[c]. [5]



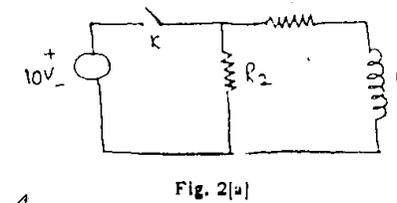Q. [2] [a] In the Fig. 2[a], find the expression for currents and voltage through the inductor L and resistance R1 and R2 after the switch is opened. Assumed steady state initial condition with the switch closed at t=(0-) [L=1H, R1=R2=10ohm] [8]



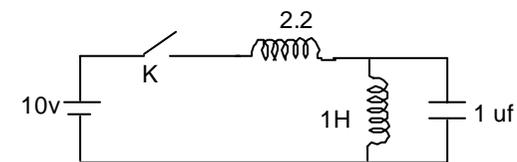[b] In the circuit in Fig. 2[b] switch k is closed and steady state condition reached. Now at time t=0. switch K is opened . Obtain the expression for the current through the inductor using Laplace transform. [8]



- Q. [3] [a] State and prove integration and derivation theorem of L.T. [4]  
 [b] State whether the system with transfer function given below is stable or not. [4]

$$H = \frac{K}{s(s+2)(s^2+3)+K}$$

- [c] The transformed current in a network is given by the following expression:

$$I(s) = \frac{5S}{(s+1)(s+3)}$$

Find the time domain current from the plot of poles and zeroes of I(s) in S-plane. [8]

- Q. [4] [a] Find the voltage transfer ratio for the network shown in Fig. 4[a]. [8]


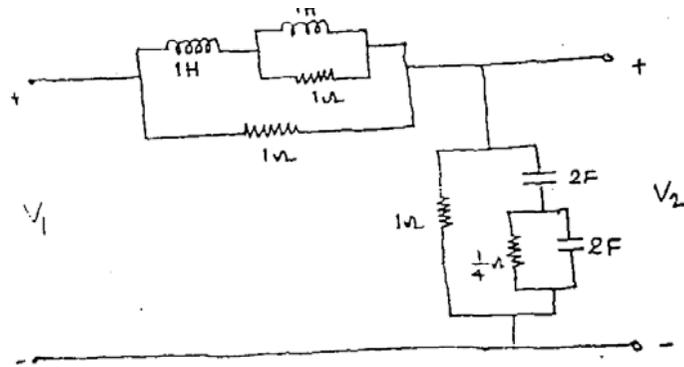


Fig. 4[a]

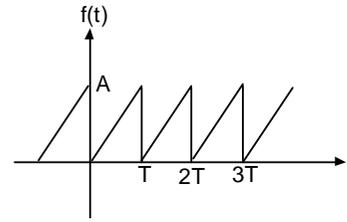- [b] Find the Fourier series expansion of the continuous wave form shown in fig. 4[b]. [8]




- Q. [5] Draw the bode plot (magnitude and phase) for the function given below: [16]  
 $H(s) = \frac{5}{s(1+0.2s)(s^2+16s+100)}$ . Use semi-log graph paper. Also discuss briefly about the plot.

- Q. [6] [a] Realize the given driving point impedance function: [6]  
 $Z(s) = \frac{4(s^2+1)(s^2+9)}{s(s^2+4)}$

- [b] For a symmetrical network prove that  $h_{22} - h_{12} h_{21} = 1$ .

Where  $h_{11}$ ,  $h_{22}$ ,  $h_{12}$ ,  $h_{21}$  are hybrid parameters of a two-port network. [4]

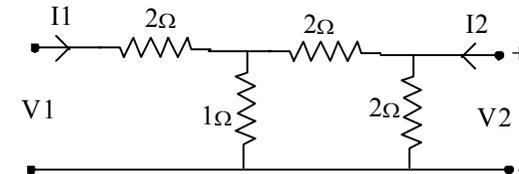- [c] Determine the z-parameter of the circuit shown in fig 6[c].




**PURBANCHAL UNIVERSITY**  
**III SEMESTER FINAL EXAMINATION-2003**  
**LEVEL:** B. E. (Computer/Electronics & Communication)  
**SUBJECT:** BEG223EL, Electrical Engineering-II  
**Full Marks:** 80  
**Pass Marks:** 32  
**TIME:** 03:00 hrs.

Candidates are required to give their answers in their own words as far as practicable.

All questions carry equal marks.

Attempt any FIVE questions

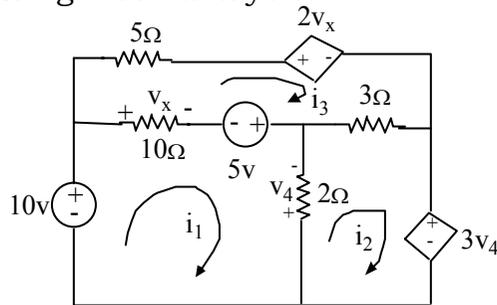
Q. [1] [a] Define passive network. Solve the given network using mesh analysis. [2+8]




[b] Calculate: [6]

- [i]  $i_1(0_+)$  [ii]  $i_2(0_+)$  [iii]  $di_1/dt(0_+)$
- [iv]  $di_2/dt(0_+)$  [v]  $d^2 i_1/dt^2(0_+)$  [vi]  $d^2 i_2/dt^2(0_+)$

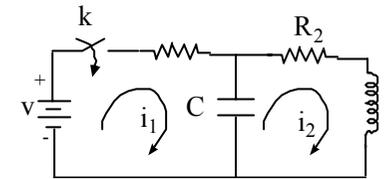
When the switch is closed at time  $t = 0$  in the circuit given below:



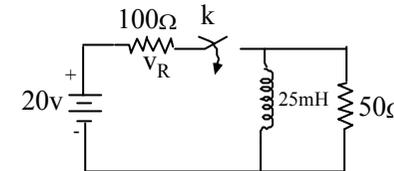Q. [2] [a] What is damping ratio? Find  $V_R$  in the circuit given below at time  $t = [a]-1 \text{ ms}; [b]0^+; [c]0.5 \text{ ms}$  [8]




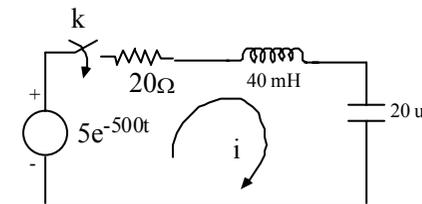[b] Solve the given network in the fig 2[b] using Laplace method. Assuming current through inductor and charge at capacitor is zero before switching. Switch is closed at time  $t = 0$ . [8]



Q. [3] [a] Find the Laplace Transformation of the first derivatives. [3].

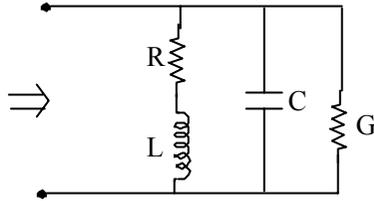
[b] Find the driving point impedance as a function of complex frequency  $s$  for the network shown in fig. 3[b]. [7]




[c] Determine the value of  $K$  for the network to be stable.

$$G(s) = \frac{k}{s(s^2 + s + 1)(s + 2) + k}$$

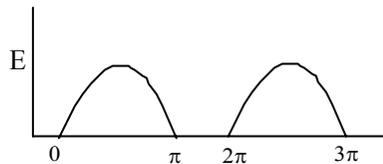Q. [4] [a] Find the Fourier series expansion of half sinusoidal wave shown in fig 4[a]. [8]



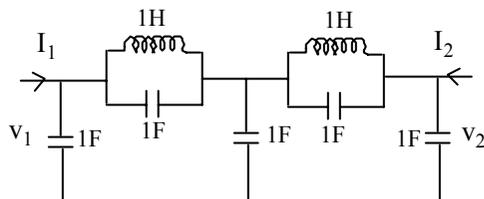[b] Find the voltage ratio transfer function  $G_{21}$ , of the circuit given below. [8]



Q. [5] Define roll-off and skirt. Sketch the asymptotic Bode plot in semi-log paper (magnitude and phase) for the network whose transfer function is given as:

$$G(s) = \frac{75(1 + 0.5S)}{S(S^2 + 16S + 100)}$$


Also discuss briefly about the plot. [3+10+3]

Q. [6] [a] synthesize the following network function:

$$Y(s) = \frac{S(S^2 + 2)(S^2 + 4)}{(S^2 + 1)(S^2 + 3)}$$

What is band stop filter? [7]

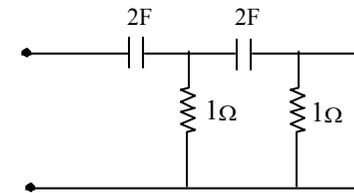[b] Find  $z$  parameter for the RC ladder network shown below. [9]



**PURBANCHAL UNIVERSITY**

**III SEMESTER BACK-PAPER EXAMINATION-2003**

**LEVEL:** B. E. (Computer/Electronics & Communication)

**SUBJECT:** BEG223EL, Electrical Engineering-II

**Full Marks:** 80

**TIME:** 03:00 hrs.

**Pass Marks:** 32

*Candidates are required to give their answers in their own words as far as practicable.*

*All questions carry equal marks. The marks allotted for each sub-question is specified along its side.*

**Attempt any FIVE questions**

Q. [1] [a] Use loop analysis to determine branch current in the network of fig. 1[a]. [8]

Figure:

[b] In the given network, the switch k is in position a for a long period of time. At t=0, the switch is moved from a to b. Find  $v_2(t)$  assume the initial current in the 2H inductor zero. [8]

Figure:

Q. [2] [a] In the given circuit, capacitor C has a initial voltage of 10 volts and at the same instant current in the inductor L is zero. Switch K is

closed at time t =0. Obtain expression for the voltage V(t) across the inductor. [8]

Figure:

[b] In the given parallel R-L-C circuit switch K is opened at time t=0. Obtain the particular solution for v(t) using Laplace transformation. [8]

Figure:

Q. [3] [a] Write down the unit step, unit ramp and unit impulse function in time domain. Also find the Laplace transformation of each spectrum. [10]

[b] In the given parallel R-L-C circuit switch k is opened at time t=0. Obtain the particular solution for V(t) using laplace transformation. [8]

Figure:

Q. [4] [a] Synthesize the network whose impedance is given as  $z(s) = \frac{9S + 20}{S^2 + 4S}$  [4]

[b] Plot the asymptotic Bode-diagram of magnitude as well as for phase for the given network function. [12]

$$G(s) = \frac{20(S + 1)}{S(S^2 + 2S + 10)(S + 5)}$$

Use semi-log paper.

Q. [5] [a] The transformed current in a network is given by the following expression:

$$I(s) = \frac{5S}{(S + 1)(S + 3)}$$

Find the time domain current from the plot of poles and zeroes of  $I(s)$  in a S-plane. [8]

[b] For the given network find the voltage ratio transfer function. [8]

Figure:

Q. [6] [a] For a reciprocal network prove that  $AD-BC=1$ . where ABCD are transmission parameters of a two-port network. [6]

[b] Find the y and z parameters for the given resistive network. [10]

Figure: